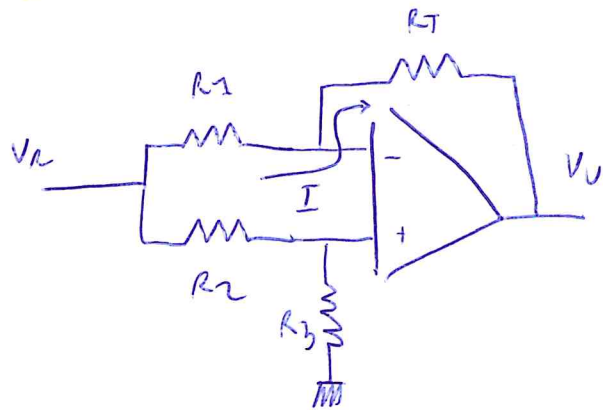


# ESERCIZIO 1



RISOLUZIONE CIRCUITO  $\rightarrow$  EQUAZIONE

$$V_U = I \left( \frac{R_1 R_3}{R_2} - R_T \right) = I (R_1 - R_T)$$

$$I = \frac{V_R}{R_1} \left( \frac{R_2}{R_1 + R_3} \right) = \frac{V_R}{2R_1} = 2 \text{ mA}$$

$$R_T^{(T)} = R_0 e^{\left( \rho \left( \frac{1}{T_S} - \frac{1}{T_0} \right) \right)} \rightarrow \text{LINEARILLO ATTORNO A } 37^\circ\text{C} \rightarrow R_L(T_S)$$

$$R_L(T_S) = R_0 e^{\left( \rho \left( \frac{1}{T_S} - \frac{1}{T_0} \right) \right)} \quad T_1 = 37^\circ\text{C}$$

$$R_1 = R_0 e^{\left( \rho \left( \frac{1}{273+37} \right) - \frac{1}{273+T_0} \right)} = 215.37^\circ\text{C}$$

$$\alpha_1 = - \frac{\rho}{(273+37)^2} = -0.0468^\circ\text{C}^{-1}$$

$$V_U = I \left( \cancel{R_1} - \cancel{R_L} - R_{L1} \alpha_1 (T_S - T_1) \right) = -I R_{L1} \alpha_1 (T_S - T_1)$$

$$R_1 = 215.37 \Omega \Rightarrow R_1 \cong R_{L1}$$

$$\Delta T = T_S - T_1$$

$$V_U = S \Delta T$$

$$S = -I R_{L1} \alpha_1 = 0.02 \text{ V/C}$$

$$\Rightarrow \Delta T = \frac{V_U}{S} = \frac{0.04}{0.02} = 2^\circ\text{C} \Rightarrow \boxed{T_S = \Delta T + T_1 = 39^\circ\text{C}}$$

$$|\text{ERRORE}| = \left| \frac{\Delta V}{S} \right| = \left| \frac{I R_1 - I R_L}{S} \right|$$

$$\Delta V = (I R_1 - I R_L) - (I R_1 - I R_T) \quad S = -I R_{L1} \alpha_1$$

$$\frac{\Delta V}{S} = \frac{-I R_L + I R_T}{I R_{L1} \alpha_1} = \frac{\Delta R}{R_{L1} \alpha_1}$$

$$\left| \frac{\Delta V}{S} \right| = \frac{R_T(39) - R_L(39)}{0.0468 \cdot 215.37} = 0.1^\circ\text{C}$$



$$R_T(39) = R_0 \cdot \rho \left( \frac{1}{273+39} - \frac{1}{273+0} \right) = 196.24 \Omega$$

$$R_L(39) = R_{L1} (1 + \alpha_1 (2)) = 195.21 \Omega$$

$$C = \frac{1}{S} = 50^\circ\text{C}/\text{V} \quad \Delta T = C V_U$$

$$32^\circ\text{C} \rightarrow \Delta T = -5^\circ\text{C} \Rightarrow V_U = -0.1\text{V}$$
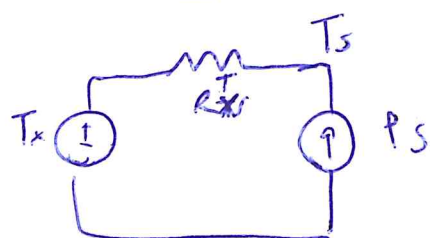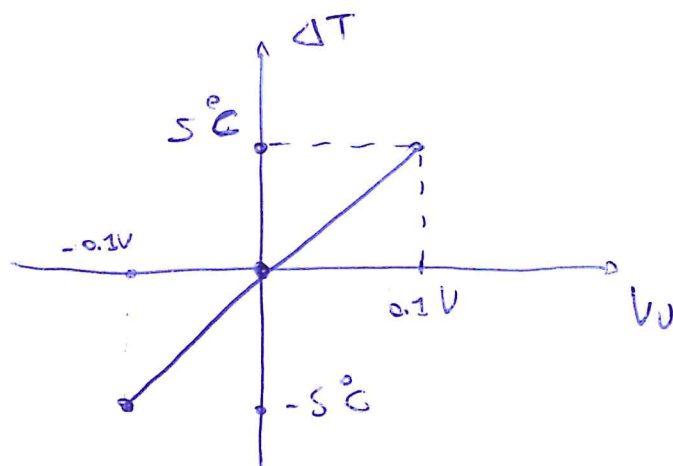
$$42^\circ\text{C} \rightarrow \Delta T = 5^\circ\text{C} \Rightarrow V_U = 0.1\text{V}$$



$$P_s = R_T(T_s) I^2$$

$$\Delta T = T_s - T_x$$

LINBAWILL ATTONNO A  $T_x = 40^\circ\text{C}$

$$R_L^2 = R_{L2} (1 + \alpha_2 (T_s - T_x))$$

$$R_{L2} = R_T(40^\circ\text{C}) = 180.40 \Omega \quad \alpha_2 = \frac{\rho}{(273+40)^2} = -0.0453^\circ\text{C}^{-1}$$

$$\Delta T = \frac{R_{T5} R_{L2} I^2}{1 - q_2 R_{T5} R_{L2} I^2} = 0.04^\circ\text{C}$$

$$T_5 = 40^\circ\text{C} + \Delta T = 40.04^\circ\text{C}$$

$$|\text{ERROR}| = \left| \frac{R_T(T_5) - R_L(T_5)}{0.0468 \cdot 215.37} \right| = 0.23^\circ\text{C}$$

$$\underline{T_{\text{measured}}} = \underline{T_5 - \Delta T} = \underline{39.81^\circ\text{C}}$$

TEORIA  $\rightarrow$  VERIFICATION

